

DIGITAL LOGIC DESIGN LAB (EET1211)

LAB III: Design, Construct & examine the Combinational Circuit to Solve a Given Problem

Siksha 'O' Anusandhan (Deemed to be University), Bhubaneswar

Branch: CSE	Section: 2341211	Subgroup No.: 7
Name	Registration No.	Signature
SURYAMADHAB MOHARANA	2341013398	Suryamadhav Mohorana

Marks: _____/10

Remarks:

Teacher's Signature

I. OBJECTIVE:

1. Design a combinational circuit with four inputs A, B, C and D and one output F. The output F value 1 when A=0 or (B=1 and C=1) or (B=1 and C=1 and D=1).
2. Design a combinational circuit with three inputs x, y and z and three outputs A, B and C. When binary input is 0, 1, 2 or 3 the binary output is two greater than the input. When the binary input 4, 5, 6 and 7, the binary output is two less than the input.
3. Design, construct, and test a circuit that generates an even parity bit from three message bits.
4. Minimize the Boolean function. Implement the Boolean function $F(A, B, C, D) = \prod M(0, 1, 4, 5, 6, 7, 8, 10, 12, 14)$ using K-map and implement the function two-level NOR gate circuit.

II. PRE-LAB :

Objective 1.

a) obtain the truth table.

Ans. $F = (A=0) \text{ or } (B=1 \text{ and } C=1) \text{ or } (B=1 \text{ and } C=1 \text{ and } D=1)$
 $= \bar{A} + BC + BCD.$
 $= \bar{A} + BC.$

A	B	C	D	\bar{A}	BC	$\bar{A} + BC$
0	0	0	0	1	0	1
0	0	0	1	1	0	1
0	0	1	0	1	0	1
0	0	1	1	1	0	1
0	1	0	0	1	0	1
0	1	0	1	1	0	1
0	1	1	0	1	1	1
0	1	1	1	1	1	1
1	0	0	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	0	0	0
1	0	1	1	0	0	0
1	1	0	0	0	0	0
1	1	0	1	0	0	0
1	1	1	0	0	1	1
1	1	1	1	0	1	1

b) Derive the boolean expression that uses the NAND gate to realize.


$$\text{Ans. } \bar{A} + BC$$

$$= \overline{\bar{A} + \bar{B}C}$$

$$= \overline{\bar{A} \cdot \bar{B}C}$$

$$= \overline{A \cdot \bar{B}C}$$

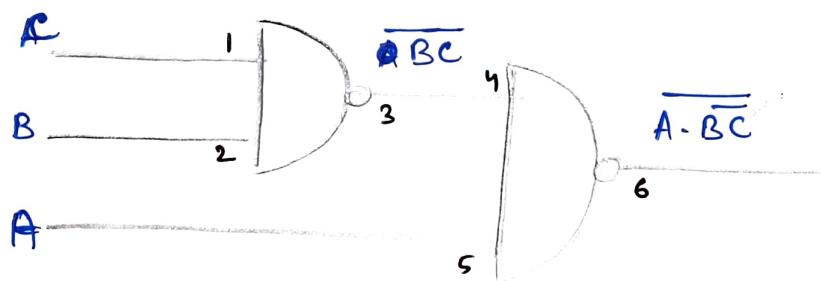c) Draw the circuit using NAND gate only.



Objectives:

a) obtain the truth table.

<u>Ans.</u>	X	Y	Z	A	B	C
0	0	0	0	0	1	0
0	0	0	1	0	1	1
0	1	0	0	1	0	0
0	1	0	1	1	0	1
1	0	0	0	0	1	0
1	0	0	1	0	1	1
1	1	0	0	1	0	0
1	1	1	1	1	0	1

b) Obtain the boolean expression using minimization technique.

Ans.

$$\begin{aligned} A &= \bar{x}yz\bar{z} + \bar{x}yz\bar{z} + xy\bar{z}\bar{z} + xy\bar{z} \\ &= \bar{x}y(\bar{z}+z) + xy(\bar{z}+z) \\ &= \bar{x}y + xy \\ &= y(\bar{x}+x) \\ &= y. \end{aligned}$$


$$\begin{aligned} B &= \bar{x}\bar{y}\bar{z} + \bar{x}\bar{y}z + x\bar{y}\bar{z} + x\bar{y}z \\ &= \bar{x}\bar{y}(\bar{z}+z) + x\bar{y}(\bar{z}+z) \end{aligned}$$

$$\begin{aligned} &= \bar{x}\bar{y} + x\bar{y} \\ &= \bar{y}(\bar{x}+x) \\ &= \bar{y} \end{aligned}$$

$$\begin{aligned} C &= \bar{x}\bar{y}z + \bar{x}yz + x\bar{y}z + xy\bar{z} \\ &= \bar{x}z(\bar{y}+y) + xz(\bar{y}+y) \\ &= \bar{x}z + xz \\ &= z(\bar{x}+x) \\ &= z. \end{aligned}$$

c) Draw the circuit using minimum no. of gates.

Ans.

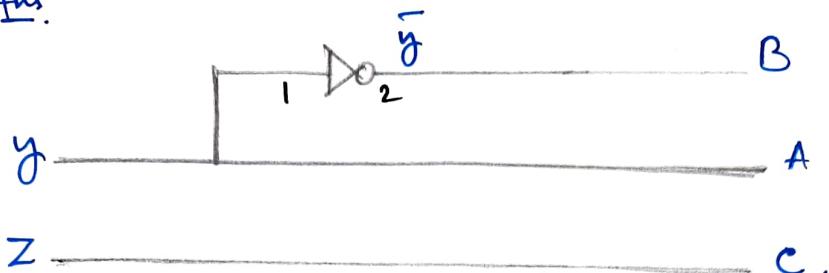

Objective 3:

a) Obtain the truth table.

Ans. $x \mid y \mid z \mid F(x,y,z)$

x	y	z	$F(x,y,z)$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1


b) Derive the boolean expression using minimization technique.

$$\begin{aligned}
 \text{Ans. } F(x,y,z) &= \bar{x}\bar{y}z + \bar{x}y\bar{z} + xy\bar{z} + xyz \\
 &= \bar{x}\bar{y}z + xyz + \bar{x}y\bar{z} + xy\bar{z} \\
 &= z(\bar{x}\bar{y} + xy) + \bar{z}(\bar{x}y + xy) \\
 &= z(x \oplus y) + \bar{z}(x \oplus y)
 \end{aligned}$$

$$\begin{aligned}
 &= z(\bar{x} \oplus y) + \bar{z}(x \oplus y) \\
 &\Rightarrow (x \oplus y) \oplus z \\
 &\Rightarrow x \oplus y \oplus z.
 \end{aligned}$$


c) Draw the circuit using minimum no. of gates.

Ans.

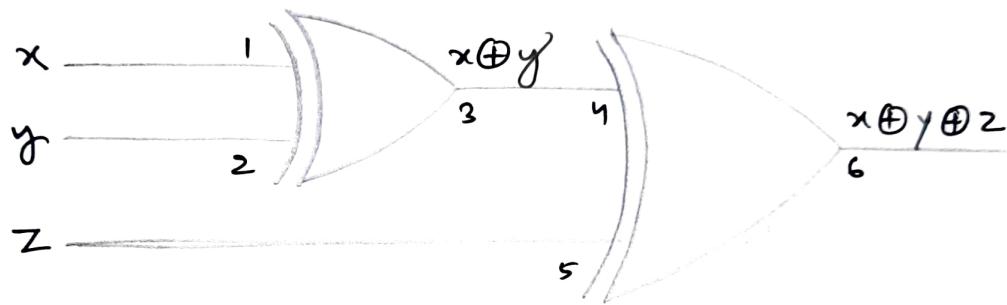

Objective 4:

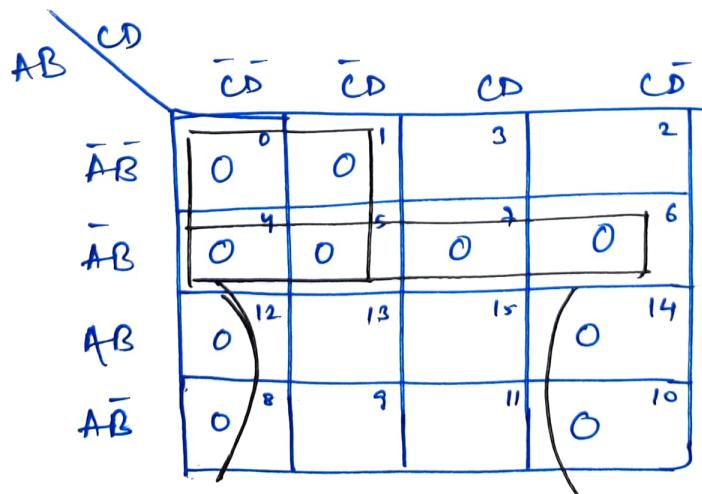a) Solve the Boolean expression using K-map.



$$\therefore \bar{F} = \bar{A}\bar{C} + \bar{A}B + A\bar{D}$$

$$\Rightarrow F = (A+C)(A+\bar{B})(\bar{A}+D)$$

b) obtain the truth table .

Ans.

A	B	C	D	\bar{A}	\bar{B}	$A+C$	$A+\bar{B}$	$\bar{A}+D$	F
0	0	0	0	1	1	0	1	1	0
0	0	0	1	1	1	0	1	1	0
0	0	1	0	1	1	1	1	1	1
0	0	1	1	1	1	1	1	1	1
0	1	0	0	1	0	0	0	1	0
0	1	0	1	1	0	0	0	1	0
0	1	1	0	1	0	1	0	1	0
0	1	1	1	1	0	1	0	1	0
1	0	0	0	0	1	1	1	0	0
1	0	0	1	0	1	1	1	1	1
1	0	1	0	0	1	1	1	0	0
1	0	1	1	0	1	1	1	1	1
01	1	0	0	0	0	1	1	0	0
1	1	0	1	0	0	1	1	1	1
1	1	1	0	0	0	1	1	0	0
1	1	1	1	0	0	1	1	1	1

c) Derive the Boolean expression that uses only NOR gate to realize.

Ans: Given: $F = (A+C)(A+\bar{B})(\bar{A}+D)$.

$$A+C = \overline{\overline{A} + C}$$


$$\bar{B} = \overline{B + B} ; A+\bar{B} = \overline{\overline{A} + \bar{B}}$$

$$\bar{A} = \overline{A+A} ; \bar{A}+D = \overline{\overline{A} + D}$$

Then:

$$\overline{\overline{A} + C} + \overline{\overline{A} + \bar{B}} + \overline{\bar{A} + D}$$

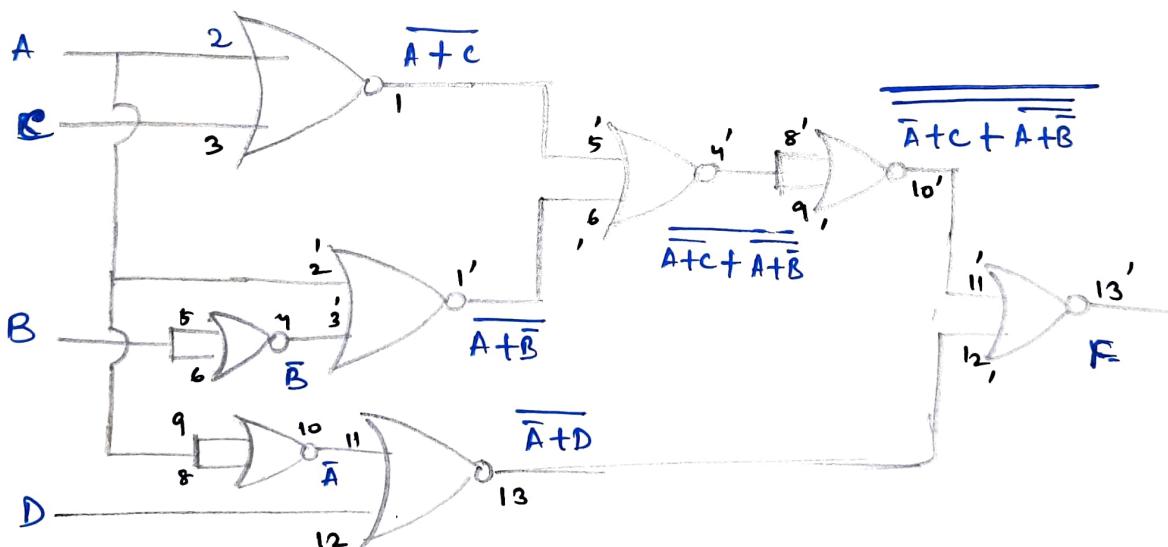d) Draw the logic gate using NOR gates only.



III. LAB :

Components required :

S/No.	Name of the Component	Specification	Quantity
1	Universal Trainer Kit	MicroLab	1
2	Connecting wires	23 SWG	As per required
3.	IC 7408	Quad 2-input AND gate	1
4.	IC 7432	Quad 2-input OR gate	1
5.	IC 7404	Hex inverter NOT gate	1
6.	IC 7400	Quad 2-input NAND gate	1
7	IC 7486	Quad 2-input XOR gate	1
8	IC 7402	Quad 2-input NOR gate	2

Observation :

7400 NAND gate :

I/P	O/P	Status
1, 2	3	
4, 5	6	
7, 10	8	
12, 13	11	Working

7486 IC (XOR gate)

I/P	O/P	status
1, 2	3	
4, 5	6	Working
10, 9	8	
13, 12	11	

7402 NOR gate

I/P	O/P	status
2, 3	1	
5, 6	4	Working
8, 9	10	
11, 12	13	

Objective 1 observation:

A	B	C	D	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1

0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

Objective 2:

x	y	z	A	B	C
0	0	0	0	1	0
0	0	1	0	1	1
0	1	0	1	0	0
0	1	1	1	0	1
1	0	0	0	1	1
1	1	0	1	0	0
1	1	1	1	0	1

Here;

$$\begin{aligned} C &= z \\ B &= \bar{y} \\ A &= y \end{aligned}$$

Objective 3 :

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Objective 4 :

A	B	C	D	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0

1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

CONCLUSION:

1) From objective 1, we conclude that for getting the output as per given instruction leads to the function:

$$\bar{A} + BC + BCD \text{ or } \bar{A} + BC.$$

which shows the required output after converting into NAND gate expression.

2) From objective 2; we conclude the output A matched with y ; output B matched with \bar{y} and output C matched with z and its verified from solving the expression.

3) From objective 3; we conclude, the even parity bit from three message bits leads to the function:

$$\cancel{x \oplus y \oplus z}$$

$$x \oplus y \oplus z.$$

4) From objective 4; we conclude NOR gate is the universal gate that can convert any Boolean expression using NOR gate.

IV Post LAB:

1. Design a combinational circuit with three inputs (x, y, z) and two outputs (F_1 and F_2). The output F_1 is 1 when binary value of the inputs is an even no. The output F_2 is 1 when binary value of input is an odd number.

Ans.

x	y	z	F_1	F_2
0	0	0	1	0
0	0	1	0	1
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	1	0
1	1	1	0	1

$$\therefore F_1 = \sum m(0, 2, 4, 6)$$

$$= \bar{x}\bar{y}\bar{z} + \bar{x}y\bar{z} + x\bar{y}\bar{z} + xy\bar{z}$$

$$= \bar{x}\bar{z}(\bar{y}+y) + x\bar{z}(\bar{y}+y)$$

$$= \bar{x}\bar{z} + x\bar{z}$$

$$= \bar{z}(\bar{x}+x)$$

$$= \bar{z}$$

$$F_2 = \sum m(1, 3, 5, 7)$$


$$= \bar{x}\bar{y}z + \bar{x}yz + x\bar{y}z + xyz$$

$$= \bar{z}(\bar{x}+x) + xz(\bar{y}+y)$$

$$\begin{aligned}
 &= \bar{x}z + xz \\
 &= z(\bar{x} + x)
 \end{aligned}$$

$\Rightarrow L$.

Circuit Diagram:

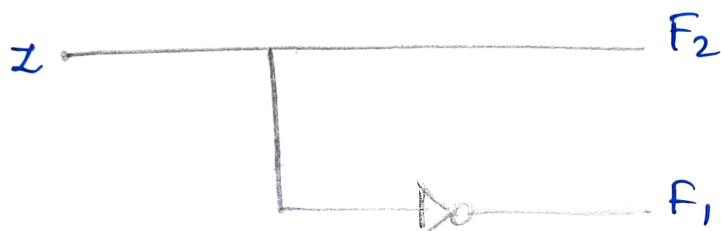

Q2. Design a 2-bit comparator circuit with two inputs (A and B) and three outputs ($A < B$), ($A = B$) and ($A > B$)

Ans.	A_1	A_0	B_1	B_0	$A < B$	$A = B$	$A > B$
	0	0	0	0	0	1	0
	0	0	0	1	1	0	0
	0	0	1	0	1	0	0
	0	0	1	1	1	0	0
	0	1	0	0	0	0	1
	0	1	0	1	0	1	0
	0	1	1	0	1	0	0

0	1	1	1	1	0	0
1	0	0	0	0	0	1
1	0	0	1	1	0	1
1	0	1	0	0	1	0
1	0	1	1	1	0	D
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	0	0	1
1	1	1	1	0	1	0

$$\begin{aligned} \therefore A \geq A < B : & \sum m(1, 2, 3, 6, 9, 11) \\ & = \bar{A}_1 \bar{A}_0 \bar{B}_1 B_0 + \bar{A}_1 \bar{A}_0 B_1 \bar{B}_0 + \bar{A}_1 \bar{A}_0 B_1 B_0 + \\ & \bar{A}_1 A_0 B_1 \bar{B}_0 + \bar{A}_1 A_0 B_1 B_0 + A_1 \bar{A}_0 \bar{B}_1 \bar{B}_0 + \\ & A_1 A_0 \bar{B}_1 B_0. \end{aligned}$$

$$\begin{aligned} A = B : & \sum m(0, 5, 10, 15) \\ & = \bar{A}_1 \bar{A}_0 \bar{B}_1 \bar{B}_0 + \bar{A}_1 A_0 \bar{B}_1 B_0 + A_1 \bar{A}_0 B_1 \bar{B}_0 + A_1 A_0 B_1 B_0 \end{aligned}$$

$$\begin{aligned} A > B : & \sum m(4, 8, 9, 12, 13, 14) \\ & = \bar{A}_1 A_0 \bar{B}_1 \bar{B}_0 + \bar{A}_1 \bar{A}_0 \bar{B}_1 \bar{B}_0 + A_1 \bar{A}_0 \bar{B}_1 B_0 + A_1 A_0 \bar{B}_1 \bar{B}_0 \\ & + A_1 A_0 \bar{B}_1 B_0 + A_1 A_0 B_1 \bar{B}_0. \end{aligned}$$