

DIGITAL LOGIC DESIGN LAB (EET1211)

LAB IV: Introduction to VHDL and Design of combinational circuits using VHDL

Siksha 'O' Anusandhan (Deemed to be University), Bhubaneswar

Branch:	Section:	Subgroup No.:
Name	Registration No.	Signature

Marks: ____/10

Remarks:

Teacher's Signature

I. Objective:

1. Design, construct, and test a Half_Adder and Half_Subtractor circuit
2. Design, construct and test a Full Adder circuit.
3. Design, construct, and test a 2 bit Parallel Adder circuit.

II. Pre-lab:

Obj. 1:

- a) Obtain the truth table.
- b) Derive the Minimized Boolean expression for each output of the circuit.
- c) Draw the logic diagram for the circuit.
- d) Write VHDL code.

Obj. 2:

- a) Obtain the truth table.
- b) Derive the Minimized Boolean expression for each output of the circuit.
- c) Draw the logic diagram for the circuit.
- d) Write VHDL code.

Obj. 3:

- a) Obtain the truth table.
- b) Derive the Minimized Boolean expression for each output of the circuit.
- c) Draw the logic diagram for the circuit.
- d) Write VHDL code.

III. LAB:

Software Required:

Observation:

(Attach screenshot of Source code, Test bench, Schematic diagram and waveform)

IV. CONCLUSION:

V. POST LAB:

1. A Half-adder is characterized by

- | | |
|---------------------------------|---------------------------------|
| a. Two inputs and two outputs | b. Three inputs and two outputs |
| c. Two inputs and three outputs | d. Two inputs and one outputs |

2. A 4-bit parallel adder can add

- | | |
|-----------------------------|----------------------------|
| a. Two 4-bit binary numbers | b. Two 2-bit binary number |
| c. Four bits at a time | d. Four bits at a time |

3. Two four bit numbers can be added using two full adders. Yes or No? Justify answer.