PLA:
(Progr

(Programmable Logic Array)

- Programmable AND, followed by programmable

* Design Fi= AB+AC+ABC

F2= (AC+BC)' vering PLA.

Any,

Product term	Enputs		outputs		
	A	В	C	FI	F ₂
A-8		D			
A-C	1		\bar{1}	1	1
ABC	0	l	1	,	<u></u>
BC	@		1)

(P.T.0)

Logic diagram:

